



# **OHM'S LAW**

# PURPOSE

- ① • Verifying Ohm's law and determining the resistances.  $R$
- ② • Calculating the equivalent resistance when we connect resistors in series  $R_1 + R_2$
- ③ • Calculating the equivalent resistance when we connect resistors in Parallel  $R_1 \parallel R_2$
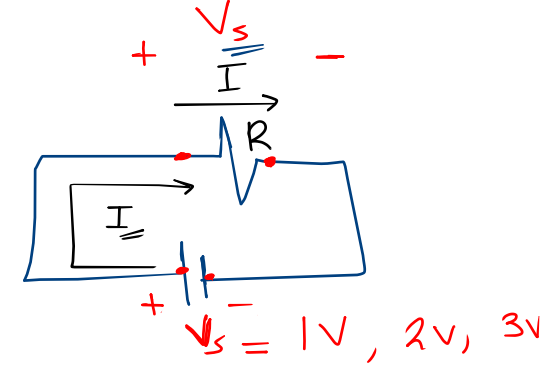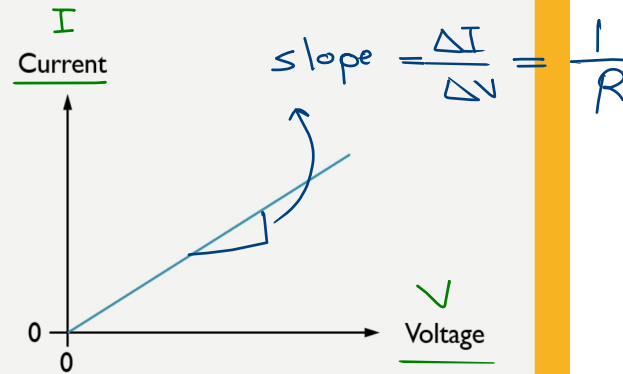
# OHM'S LAW


- For some materials, the resistance is constant no matter how much voltage is applied across it. These materials are said to obey Ohm's Law.
- Since the resistance (R) is constant, a plot of voltage (V) vs. current (I) yields a straight line for these materials.
- Notice that resistance is always the ratio of voltage across a device to the current through the device. But the resistance is constant only for those materials that obey Ohm's law.



$R \rightarrow$  Constant  
ohm's Law  
 $V = IR$

$$\text{slope} = \frac{1}{R}$$
$$R = \frac{1}{\text{slope}}$$

# OHM'S LAW

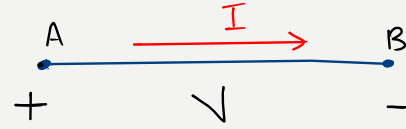

$$V \propto I$$

$$V = \text{Constant} \cdot I$$

$$V = RI$$

- Ohm's law states that the current through a conductor between two points is directly proportional to the voltage

$$\underline{V = I \cdot R}$$

Voltage (V) = current (A) × resistance (Ω)

*volt* (pointing to V), *ohm* (pointing to Ω), *Amperes* (pointing to A)

V is the voltage measured across the conductor in units of volts (V),  
I is the current through the conductor in units of amperes (A),  
R is the resistance of the conductor in units of ohms (Ω).

التوالي

## SERIES-CONNECTED RESISTORS

Current

$$I = I_1 = I_2$$


Voltage

$$V = V_1 + V_2$$


$$IR_{eq} = I_1R_1 + I_2R_2$$

Equivalent Resistor

$$R_{eq} = R_1 + R_2$$

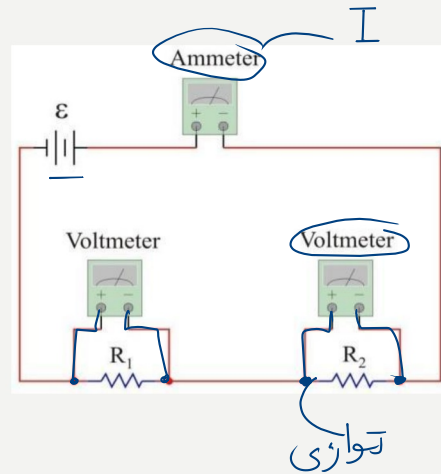

$$R_{eq} = R_1 + R_2$$

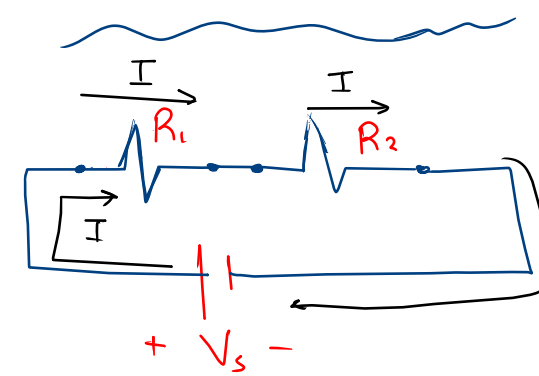

$$V_s = V_{R_1} + V_{R_2}$$

$$I = I_1 = I_2$$

$$\cancel{I}R_{eq} = \cancel{I}R_1 + \cancel{I}R_2$$

$$R_{eq} = R_1 + R_2$$

# PARALLEL-CONNECTED RESISTORS

Current

$$I = I_1 + I_2$$



Voltage

$$V = V_1 = V_2$$

$$\frac{I}{R_{eq}} = \frac{I_1}{R_1} + \frac{I_2}{R_2}$$

Equivalent Resistor
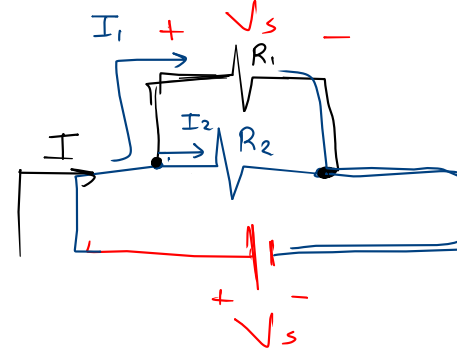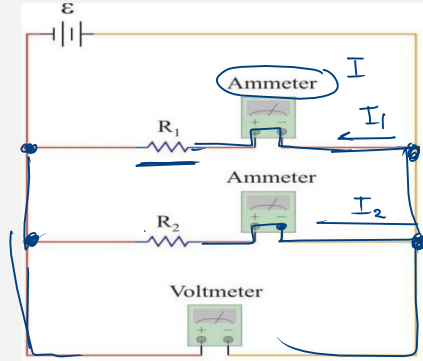
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$



$$V_s = V_{R_1} = V_{R_2}$$

$$I = I_1 + I_2$$

~~$$\frac{V_s}{R_{eq}} = \frac{V_s}{R_1} + \frac{V_s}{R_2}$$~~

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$V = IR$$

$$I = \frac{V}{R}$$

if we have only Two resistors

$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

# TOOLS

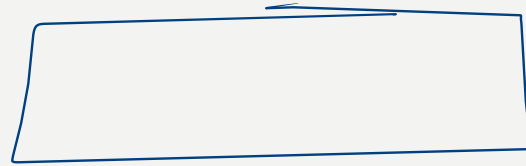

DC Power supply.


Circuits Experiment Board

Wires

Voltmeter

Ammeter

Different resistors

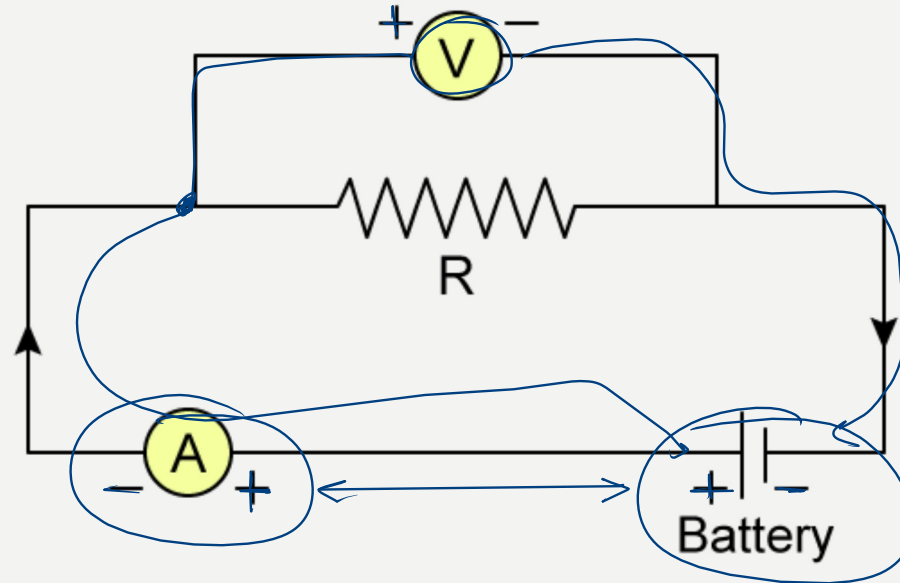



# RESULTS: PART I

**mA**  $\div 1000$  or  $\times 10^{-3}$  **A**

V (v)	$I \times 10^{-3}$ (A)	$R (\Omega) = \frac{V}{I}$
1	2	$\frac{1}{2 \times 10^{-3}} = \square$
2	~	~
3	~	~
4	~	~
5	~	~
$R_{avg} =$		

$$R_{avg} = \frac{R + R + R + R + R}{5}$$

$$\approx 1k\Omega$$

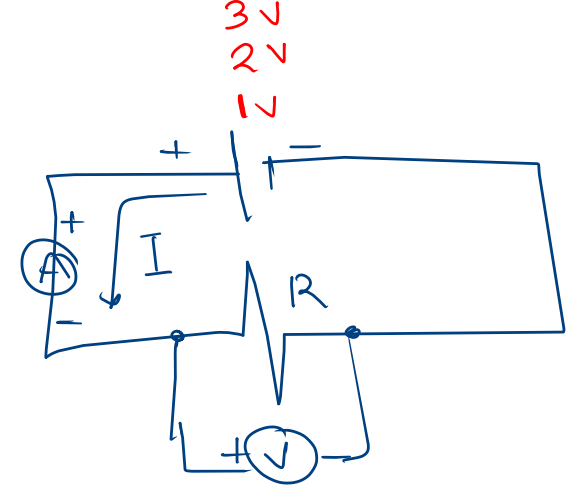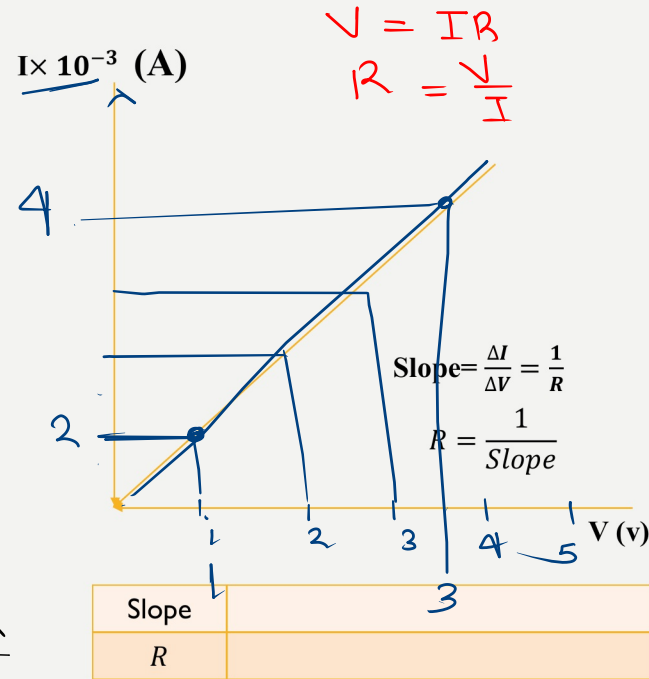

$$\text{slope} = \frac{\Delta I}{\Delta V} = \frac{(4-2) \times 10^{-3}}{3-1} = 1 \times 10^{-3}$$

$$R = \frac{1}{\text{slope}} = 1k\Omega$$

# PART II

## DETERMINED $R_{eq}$ EXPERIMENTALLY (SERIES)

$$V = IR$$

$$R = \frac{V}{I}$$

Theoretically

Calculated

$$R_1 = 220 \Omega$$

$$R_2 = 470 \Omega$$

$$R_{eq} = R_1 + R_2 \\ = 470 + 220 = 690 \Omega$$

$$\%Error = \frac{|R_{ave} - R_{eq}|}{R_{eq}}$$


نسبة الخطأ

Resistance $R=V/I$	Current <b>A</b>	Voltage <b>V</b>
~	$\times 10^{-3}$	1V
~	$\times 10^{-3}$	2V
~		~

$$R_{ave} = \frac{R+R+R+R}{4} = \square$$

$$700 \Omega$$
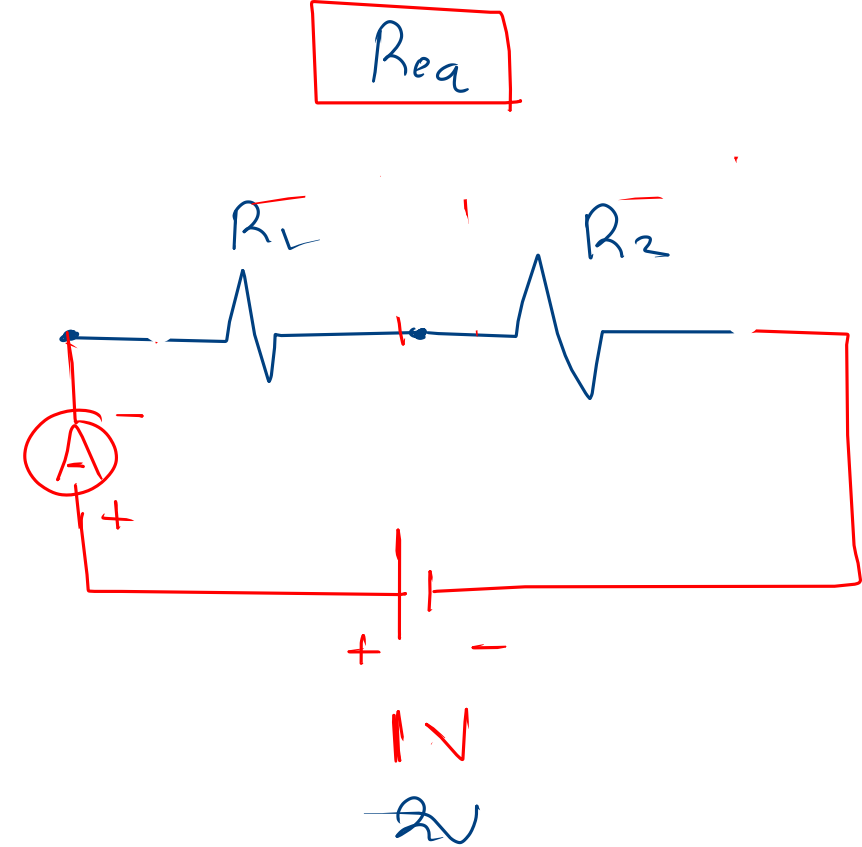
$$\frac{700 - 690}{690} = \frac{10}{690} = \square \%$$



# PART III

## DETERMINED $R_{eq}$ EXPERIMENTALLY (PARALLEL)

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \boxed{\phantom{000}}$$

$$R = \frac{V}{I}$$

### Theoretically

$$R_1 = 220 \, \Omega$$







$$R_2 = 470 \, \Omega$$

$$R_{eq} = R_1 R_2 / (R_1 + R_2)$$

$$= \frac{470 \times 220}{470 + 220} = \boxed{149.85 \, \Omega}$$

$$\% \text{Error} = \frac{|R_{ave} - R_{eq}|}{R_{eq}}$$

### Calculated

Resistance $R = V/I$	Current A	Voltage V
	 $\times 10^{-3}$	1V
	 $\times 10^{-3}$	2V
		3V
$R_{ave} = \boxed{\phantom{000}}$		

